

Lab 8

To Practice Binary to Gray Code & BCD to Excess-3 Conversion

Note: You may draw all the logic diagrams with hand and paste the pictures here. Also, the conversions in the tasks can be done by hand if doing it in soft seems difficult to you.

*Use Logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable. In logicly, use **"text"** label to point out/show all your inputs & outputs.*

Task 1

- a) Convert the given binary codes into respective gray codes. Mention each step while converting the codes.

1111, 1101, 1001, 010, 011, 110

Task #1

(a) Convert given binary Codes into gray codes.

(i) 1111
Soln:

$\Rightarrow 1 \ 1 \ 1 \ 1$

$\begin{array}{c} \oplus \quad \oplus \quad \oplus \\ \boxed{1 \ 0 \ 0 \ 0} \end{array}$ Ans

\Rightarrow "Put same element for gray code (MSB) and do Ex-OR with another element"

$\therefore \left. \begin{array}{l} \phi_3 = b_3 \\ \phi_2 = b_3 \oplus b_2 \\ \phi_1 = b_2 \oplus b_1 \\ \phi_0 = b_1 \oplus b_0 \end{array} \right\} \rightarrow \text{Steps}$

(ii) 1101
Soln:

$\begin{array}{c} 1 \ 1 \ 0 \ 1 \\ \oplus \quad \oplus \quad \oplus \\ = \boxed{1 \ 0 \ 1 \ 1} \rightarrow \text{Ans} \end{array}$

(iii) 1001
Soln:

$\begin{array}{c} 1 \ 0 \ 0 \ 1 \\ \oplus \quad \oplus \quad \oplus \\ = \boxed{1 \ 1 \ 0 \ 1} \rightarrow \text{Ans} \end{array}$

(iv) 010
Sum

5 010

~~+~~ ~~+~~

5 011
Ans

(v) 011
Sum

011

~~+~~ ~~+~~

5 010
Answer

(vi) 110
Sum

> 110

~~+~~ ~~+~~

101
Answer

b) Convert the given gray codes into respective binary codes. Mention each step while converting the codes.

1011, 0101, 1100, 0100

Convert Gray Code into binary Code:

Q 1011
Soln.

1 0 1 1
⊗/⊗/⊗/
= 1 1 0 1
Ans

Steps $\left\{ \begin{array}{l} \Rightarrow b_3 = g_3 \\ b_2 = g_3 \oplus g_2 \\ \Rightarrow b_1 = g_2 \oplus g_1 \\ \Rightarrow b_0 = g_1 \oplus g_0 \end{array} \right.$

(ii) 0101
Soln.

= 0 1 0 1
⊗/⊗/⊗/
= 0 1 1 0

= 0 1 1 0
Answer

(iii) 1100
Soln.

= 1 1 0 0
⊗/⊗/⊗/
= 1 0 0 0

Answer

(iv) 0100
Soln.

= 0 1 0 0
⊗/⊗/⊗/
= 0 1 1 1
= 0 1 1 1 Answer

Task 2

Devise a truth table for 3-bit Binary to Gray code converter. Write simplified logical expressions and simulate the logic diagram in Logically software to verify your results. Show KMap simplification as well.

a) Truth Table

Truth Table

b_2	b_1	b_0	g_2	g_1	g_0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

b) Boolean Expression (Simplified using KMap)

K-map of G_1

A \ BC	00	01	11	10
	0			
1	1	1	1	1

Expression = A

K-map of C_1

A \ BC				
	00	01	11	10
0			1	1
1	1	1		


$$\text{Expression} = A\bar{B} + \bar{A}B = A \oplus B$$

K-map of C_2

A \ BC				
	00	01	11	10
0		1		1
1		1		1

$$\begin{aligned} \text{Expression} &= \bar{B}C + B\bar{C} \\ &= B \oplus C \end{aligned}$$


c) Logic Diagram

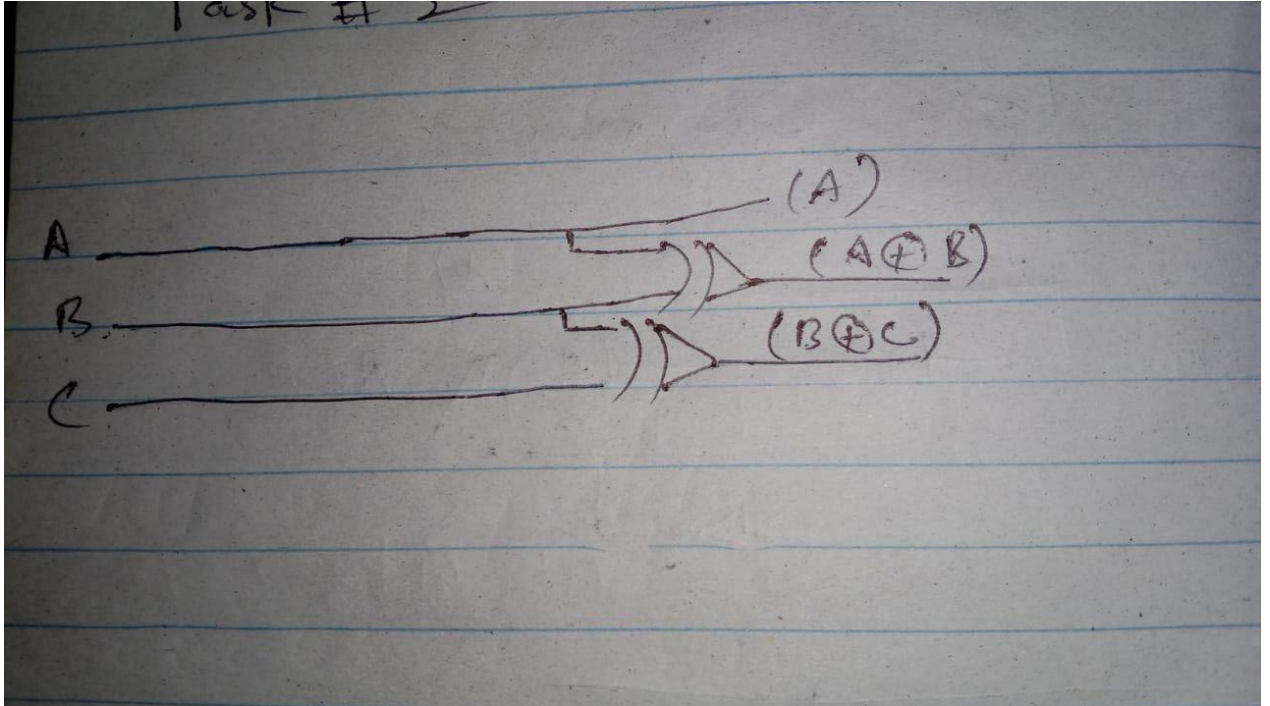

a) Software Simulation (Show here your results for a few combinations to verify the circuit)


<https://logic.ly/demo/Muzamil/p200108/2D-1>

mail YouTube Maps Flex | Student Google Account WhatsApp SLATE : My Worksp... C++ Lab Assignme... Programiz: Learn to...

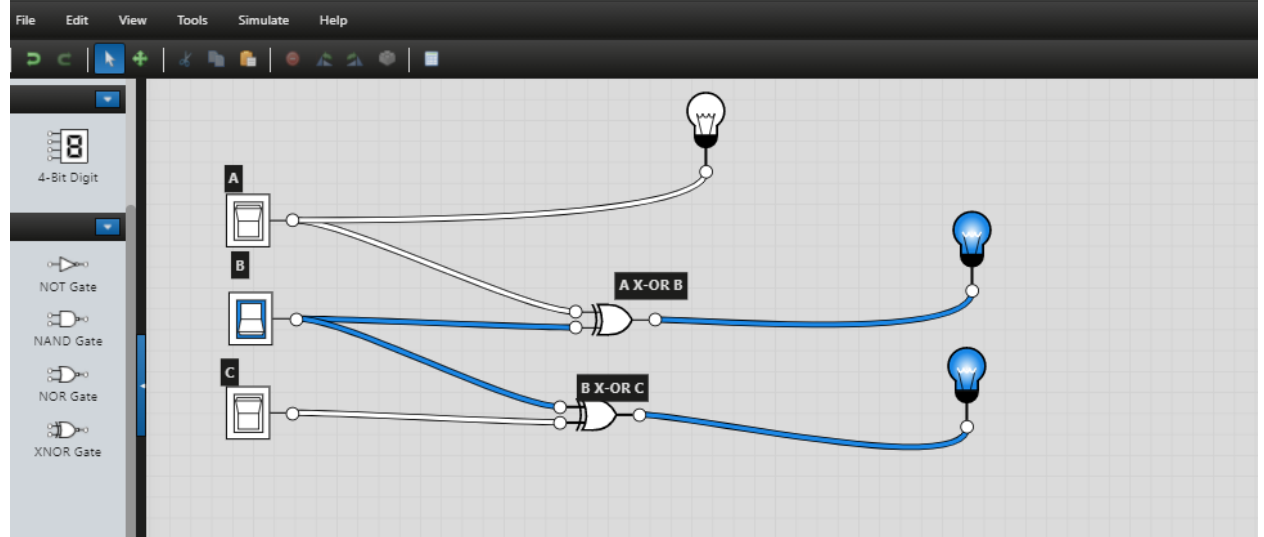

<https://logic.ly/demo/Muzamil/p200108/2D-1>


mail YouTube Maps Flex | Student Google Account WhatsApp SLATE : My Worksp... C++ Lab Assignme... Programiz: Learn to...

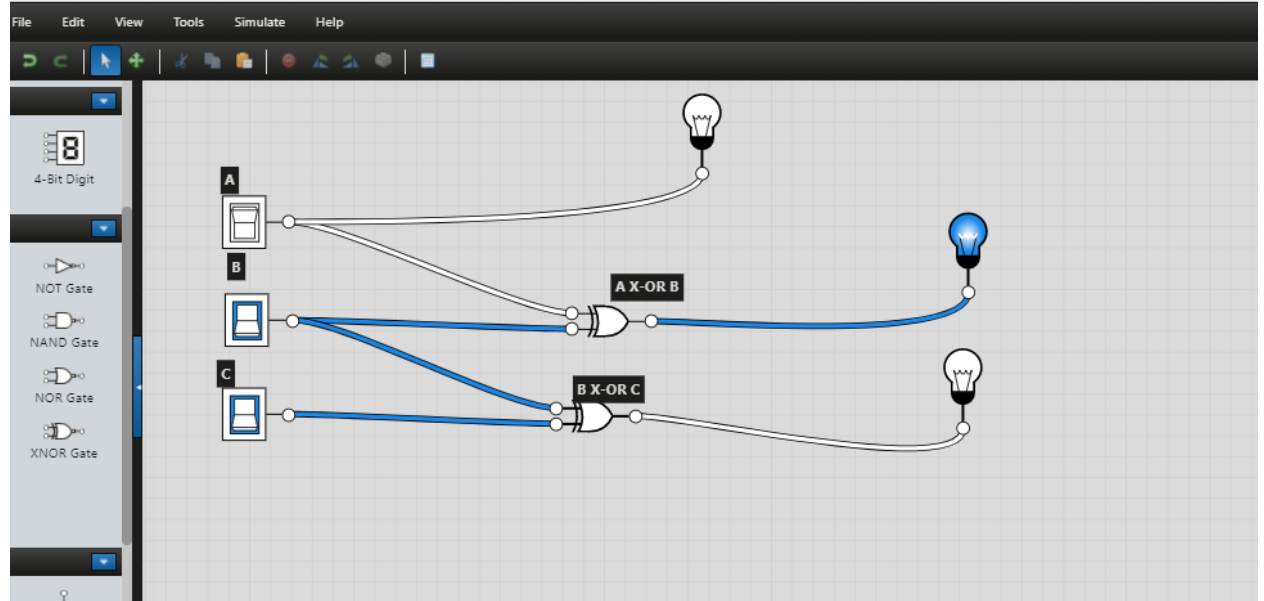

Task 3

a) For the given numbers, find excess-3 codes. Mention all the steps of conversion.

4, 9, 25, 50, 250, 405.

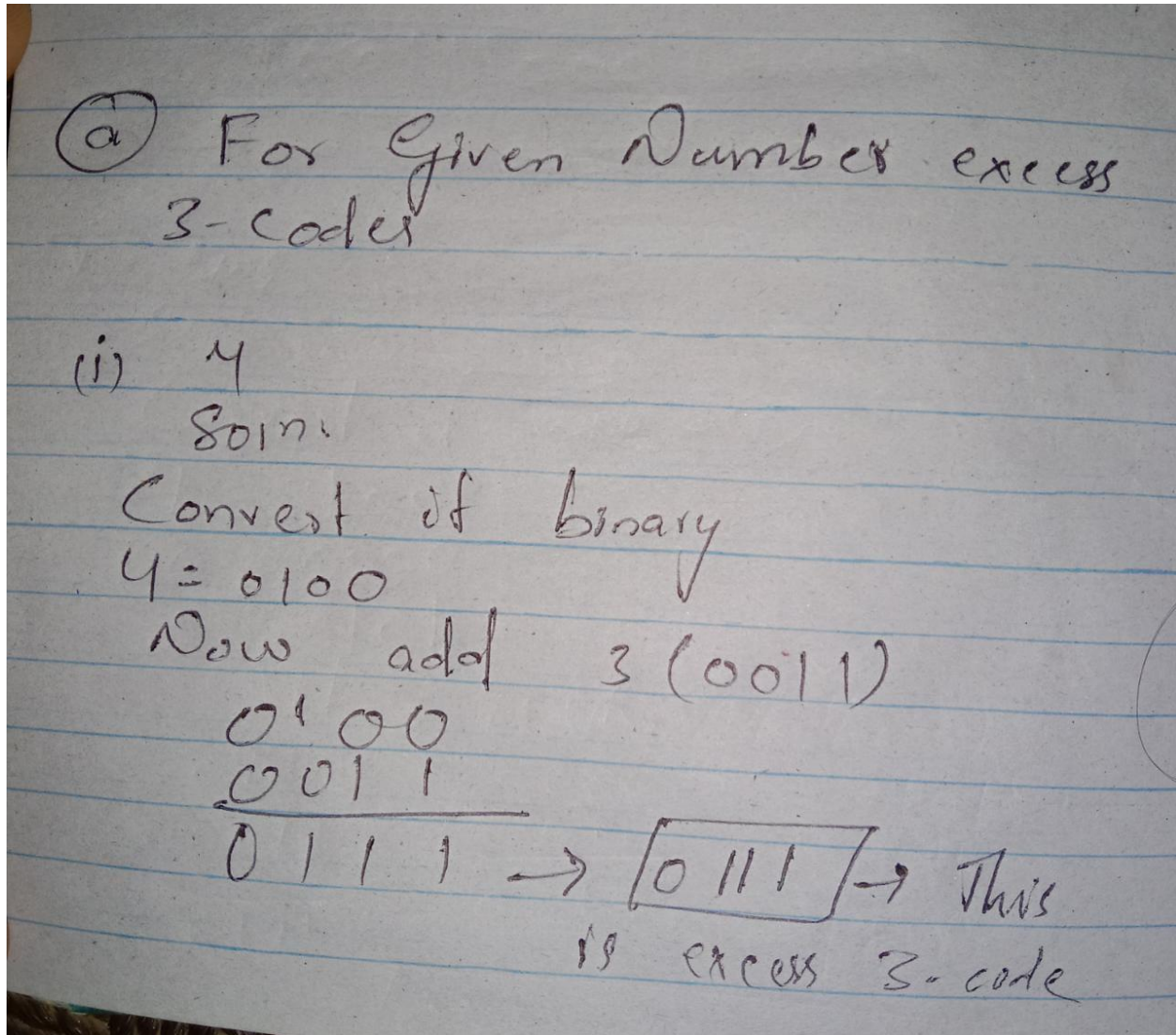

9
Given.

Convert it into BCD

$$9 = 1001$$

Now add 3

$$\begin{array}{r} 1001 \\ + 0011 \\ \hline \end{array}$$

$$1100 \rightarrow$$

$$\boxed{1100} \rightarrow \text{This}$$

is excess-3

(11) 25

Given

Convert it into BCD (separately)

$$25 =$$

$$2 = 0010$$

$$5 = 0101$$

Now add (+3) Separately

$$2 \rightarrow 0010$$

$$+ 0011$$

$$\hline 0101$$

$$5 \rightarrow 0101$$

$$+ 0011$$

$$\hline 1000$$

$$\boxed{01011000} \rightarrow \text{This is excess-3}$$

(iv) 50

Soln

Convert it into BCD (separately)

50

$$\Rightarrow 5 = 0101$$

$$0 = 0000$$

Add 3 Separately

$$\begin{array}{r} 0000 \\ + 0011 \\ \hline 0011 \end{array} \quad \begin{array}{r} 0101 \\ + 0011 \\ \hline 1000 \end{array}$$

$$= \boxed{00111000} \text{ Answer}$$

(v) 405

Soln

Convert it into BCD (separately)

$$\Rightarrow 4 = 0100$$

$$0 = 0000$$

$$5 = 0101$$

5 (Add 3 with All three)

$$\begin{array}{r} 0100 \\ + 0011 \\ \hline 0111 \end{array} \quad \begin{array}{r} 0000 \\ + 0011 \\ \hline 0011 \end{array} \quad \begin{array}{r} 0101 \\ + 0011 \\ \hline 1000 \end{array}$$

$$= \boxed{011100111000} \text{ Answer}$$

- b) Devise a truth table for BCD to Excess-3 conversion (as discussed in the lecture). Write simplified expressions and simulate the logic circuit in Logically software to verify your truth table. You may paste screenshots of a few combinations from the truth table to check your circuit. Show your KMap simplification as well.

BCD to Excess-3 Converter

b) Truth Table

BCD				Excess-3			
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	0	1	1	1	0	1
0	0	1	0	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

c) Boolean Expression (Simplified Using KMap)

K-map of w

AB \ CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$w = A + BD + Bc$$

K-map of x

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$x = \bar{B}D + \bar{B}c + B\bar{C}\bar{D}$$

K-map of V

AB	CD			
	00	01	11	10
00	1		1	
01	1		1	
11	X	X	X	X
10	X		X	X


$$Y = \bar{C}\bar{D} + CD$$

K-map for Z



AB	CD			
	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1			X


$$Z = \bar{D}$$

d) Logic Diagram

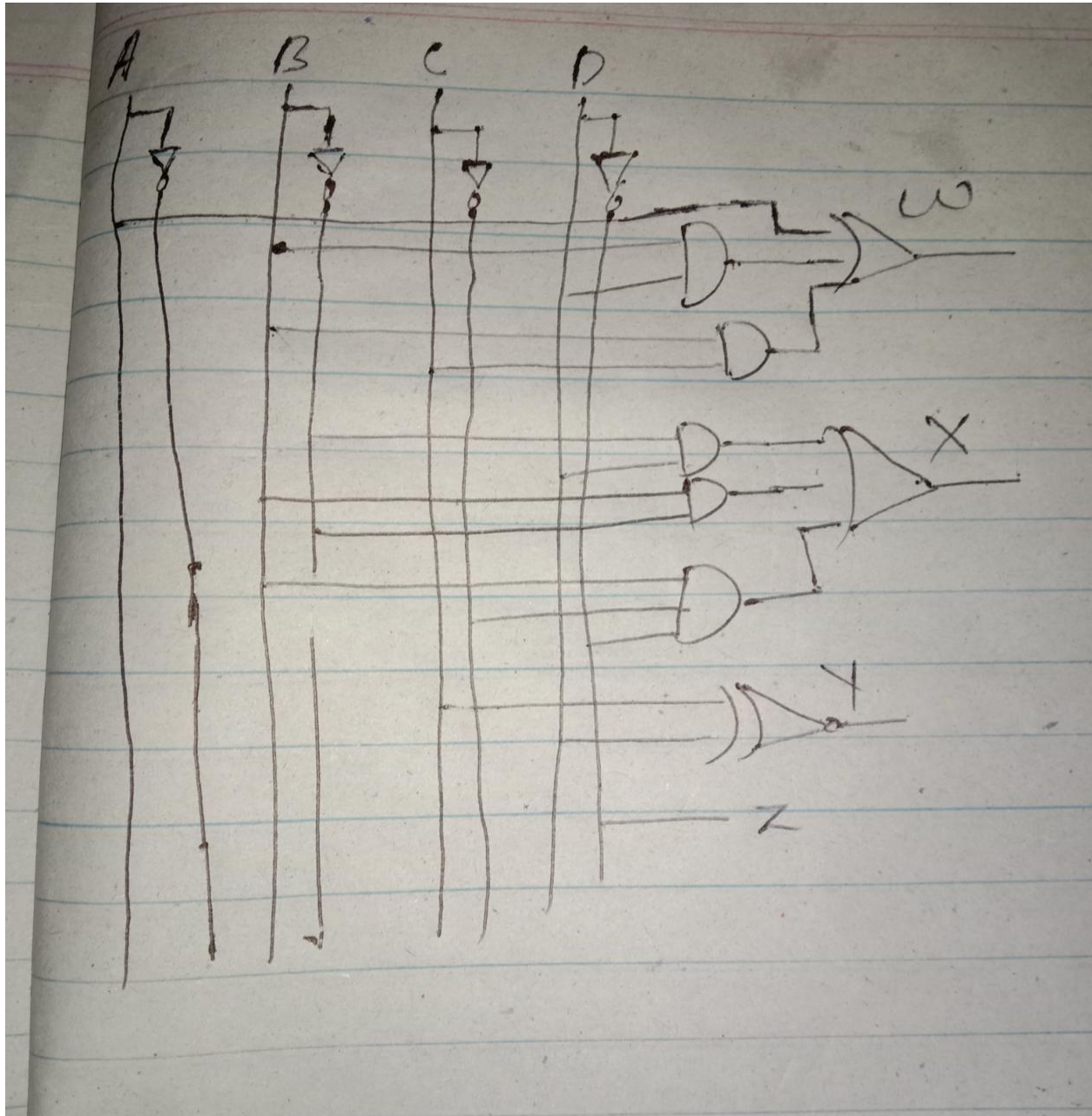

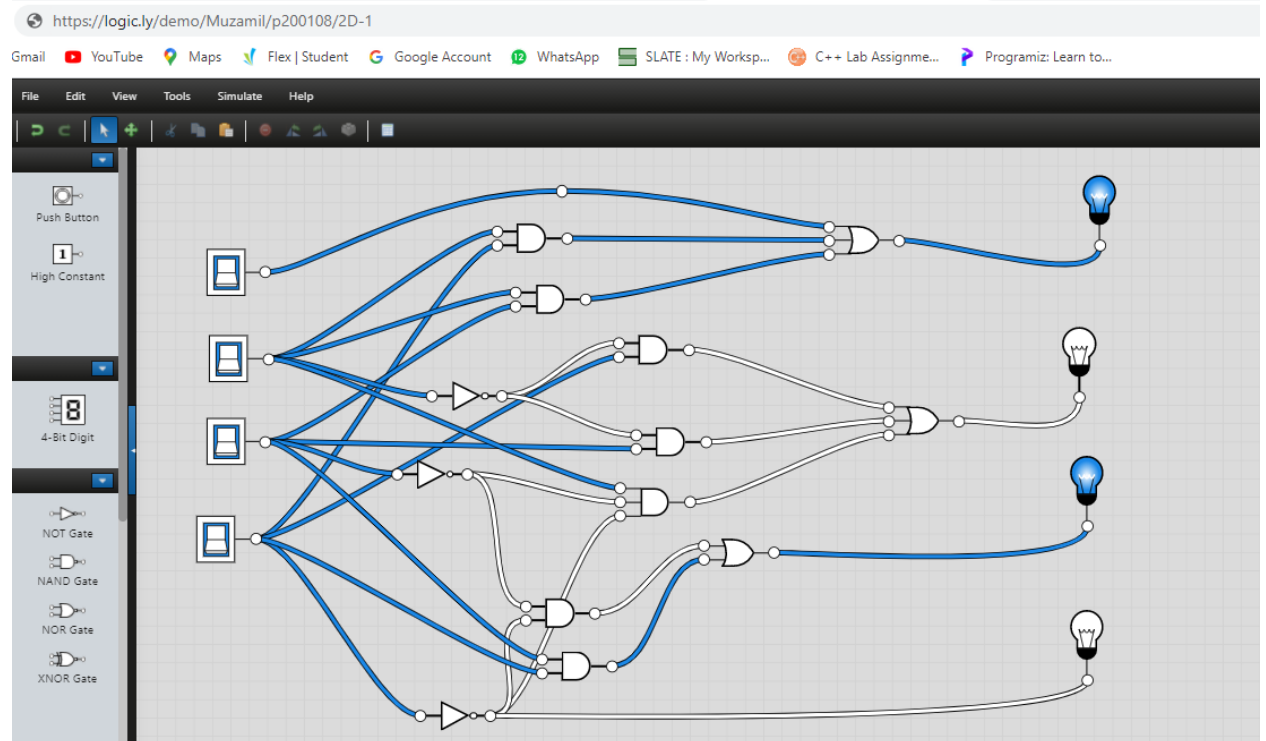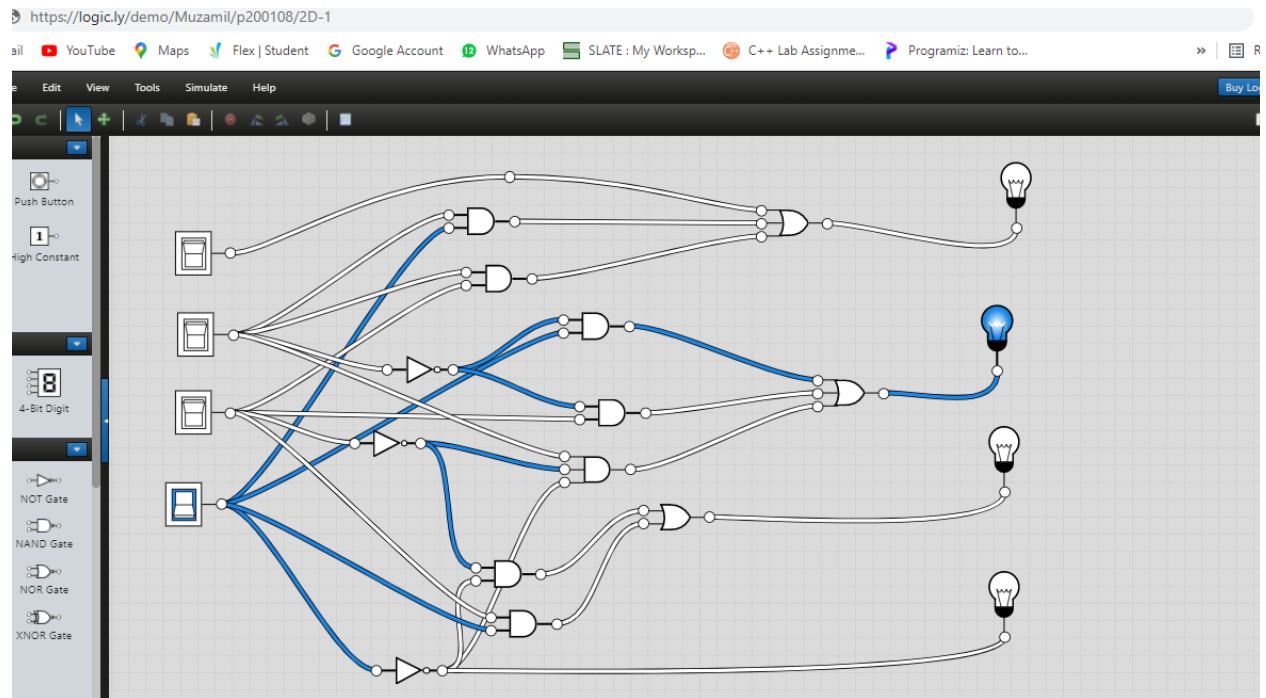e) Software Simulation (Show here your results for a few combinations to verify the circuit)



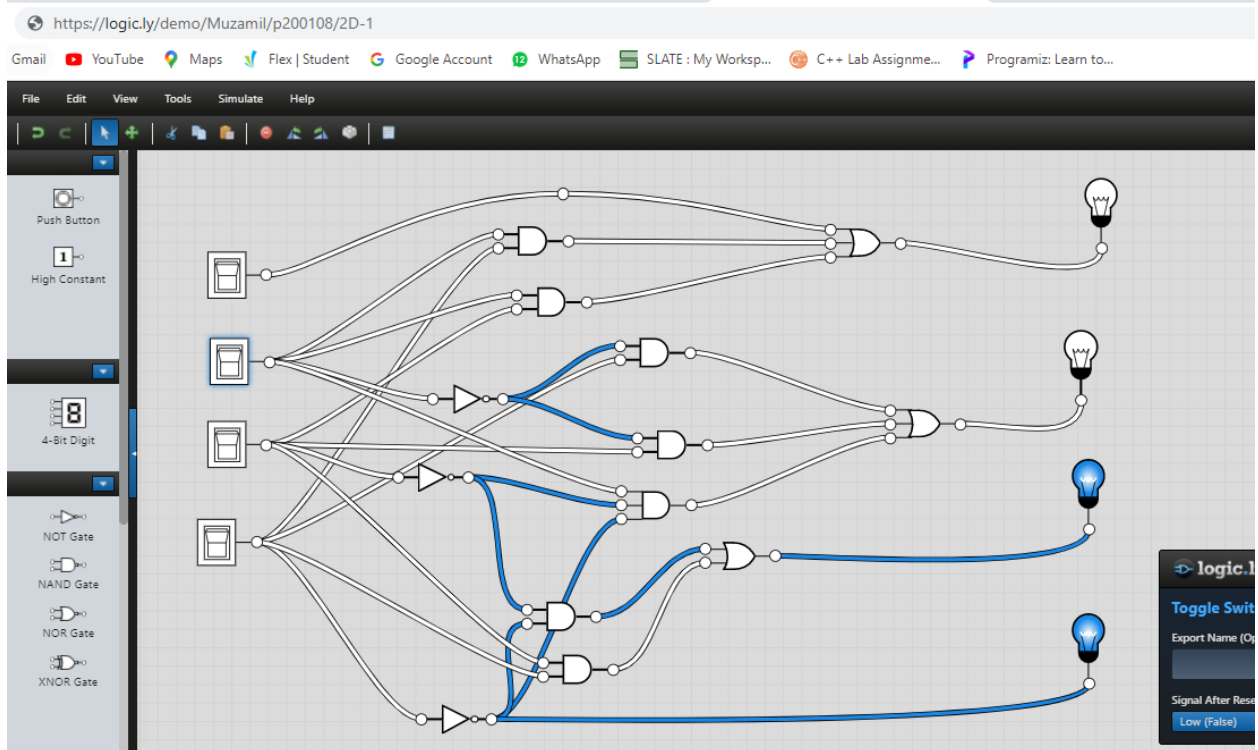

Muzamil
P20-0108
2D-1

