

## Lab 13

### To Explain the Types and Working of Digital Counters and Implement Binary Counter Using IC


Note: For all the circuits in the tasks, your logic diagrams should be either hand drawn or from the software logically. Keep them neat and legible. These circuits will be having many connections so, for simulations, make sure that you label the inputs and outputs clearly. Use Label tag in “logically”. You can also edit the pictures of your outputs in “paint” easily.

#### Tasks

1. Construct a logic circuit for 4-bit Asynchronous Counter using JK Flip Flop. Simulate your circuit to verify the outputs.

#### 4-Bit Asynchronous Counter Using JK Flip Flop

- a) Logic Diagram

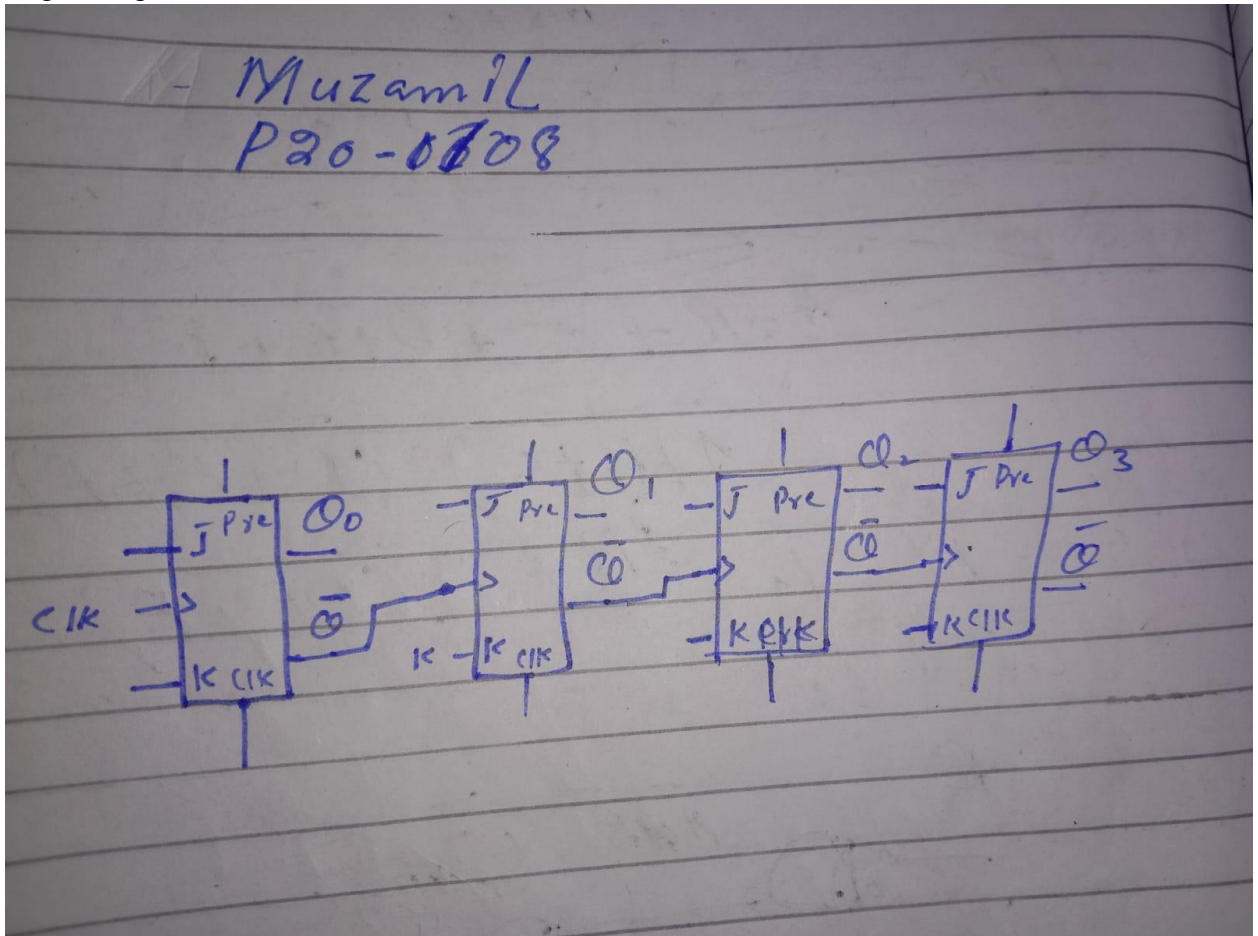


b) Truth Table

The inputs J and K are 1


Clock	Q3	Q2	Q1	Q0
1	0	0	0	0
2	0	0	0	1
3	0	0	1	0
4	0	0	1	1
5	0	1	0	0
6	0	1	0	1
7	0	1	1	0
8	0	1	1	1
9	1	0	0	0
10	1	0	0	1
11	1	0	1	0
12	1	0	1	1
13	1	1	0	0
14	1	1	0	1
15	1	1	1	0
16	1	1	1	1

c) Software Simulation

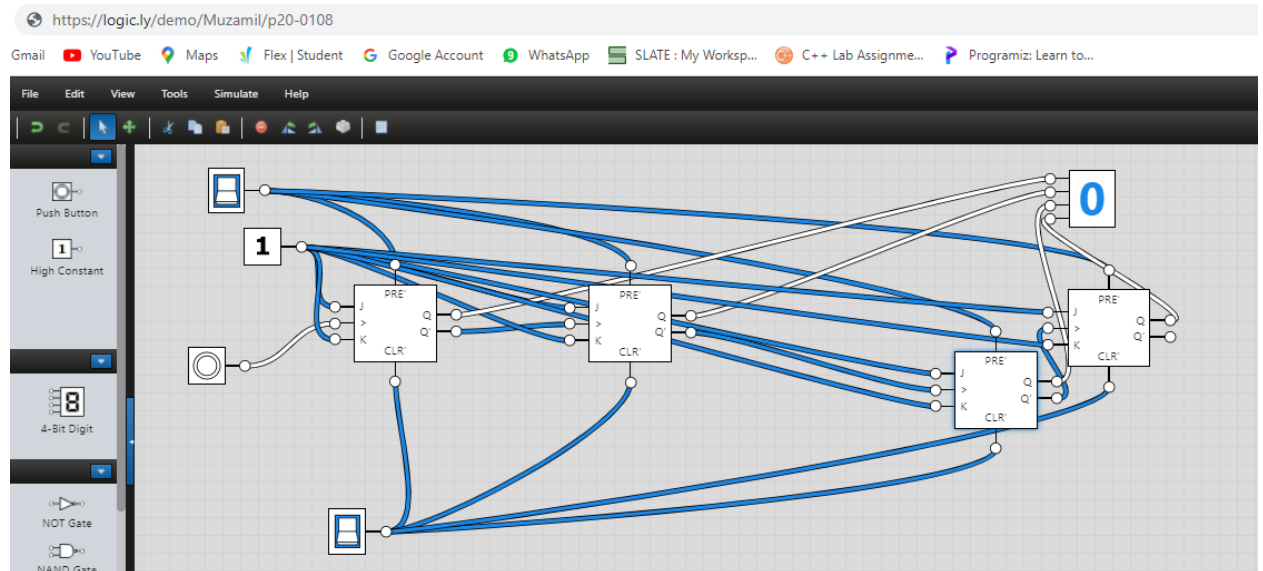


https://logic.ly/demo/Muzamil/p20-0108


mail YouTube Maps Flex | Student Google Account WhatsApp SLATE : My Worksp... C++ Lab Assignme... Programiz: Learn to...

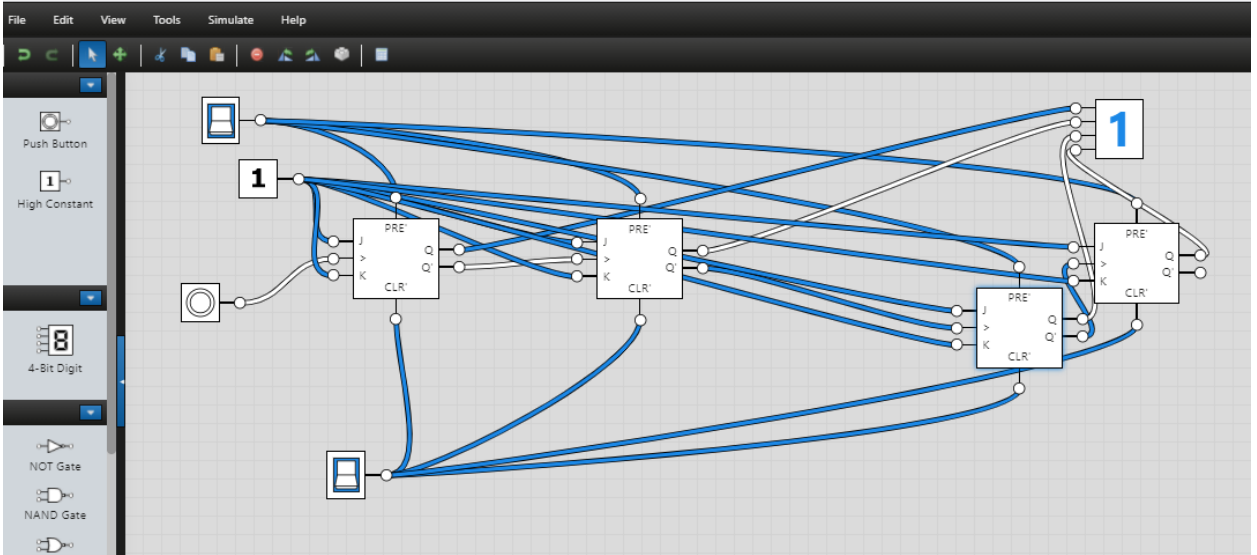

https://logic.ly/demo/Muzamil/p20-0108

mail YouTube Maps Flex | Student Google Account WhatsApp SLATE : My Worksp... C++ Lab Assignme... Programiz: Learn to... Buy Logic

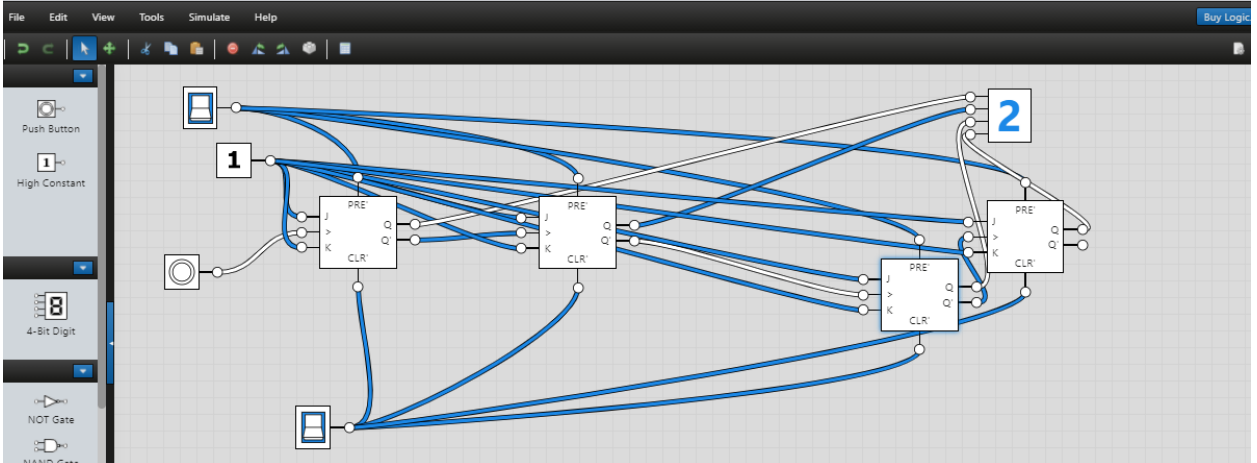


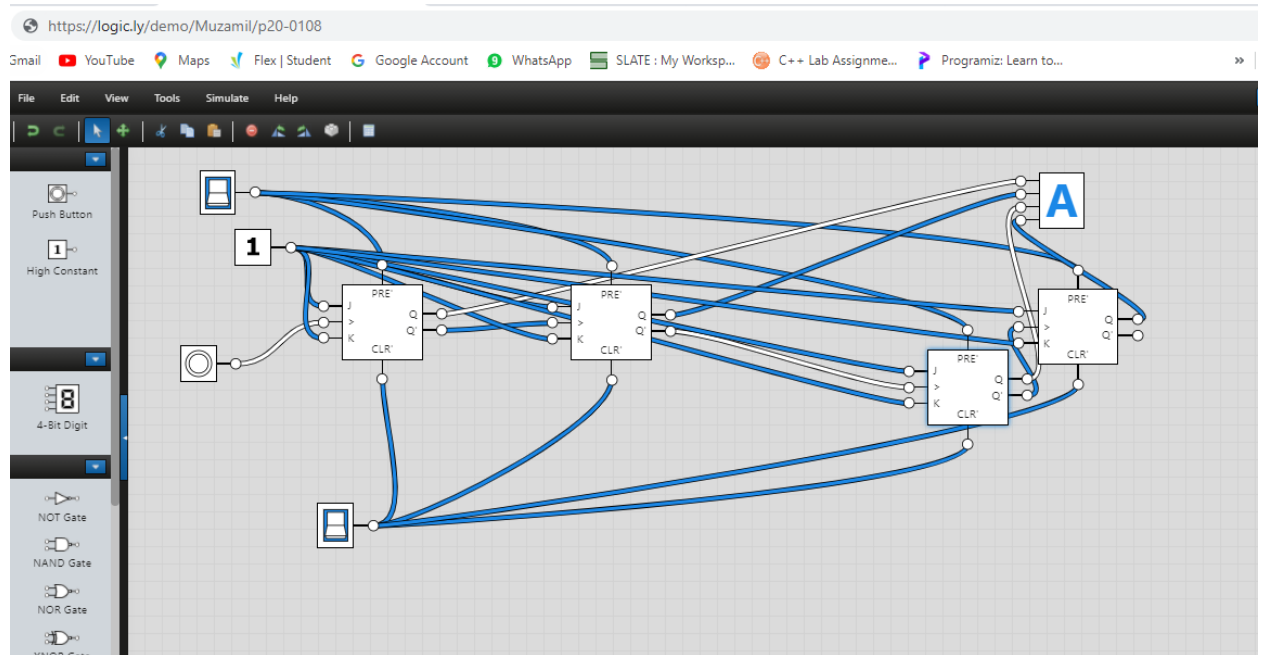

**2. Construct a logic circuit for 3-bit Synchronous Counter using JK Flip Flop. Simulate your circuit to verify the outputs.**

**a) Logic Diagram**

Muzamil  
P20-0708

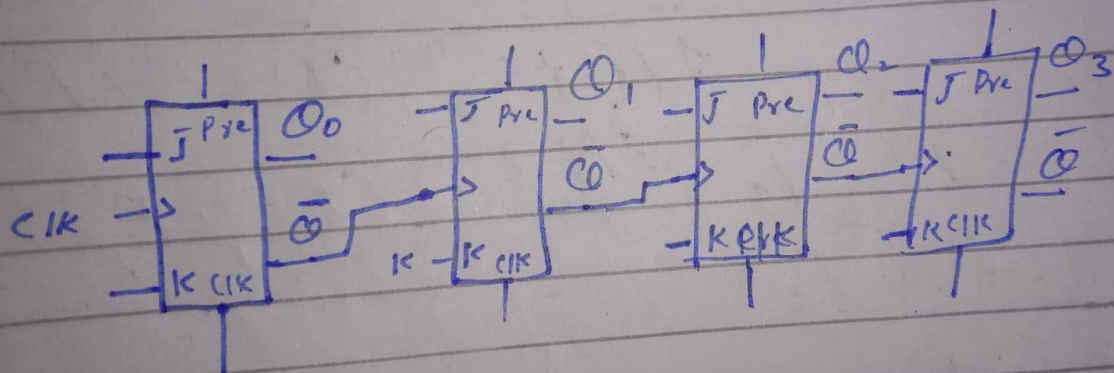

b)

c) Truth Table

J2	k2	J1	K1	J0	K0	Q2	Q1	Q0
1	X	1	X	0	X	0	0	0
1	X	0	X	X	1	0	0	1
0	X	X	0	1	X	0	1	0
0	X	X	1	X	1	0	1	1
X	0	0	X	1	X	1	0	0
X	1	1	X	X	1	1	0	1
X	0	X	0	1	X	1	1	0
X	1	X	1	X	0	1	1	1

d) Software Simulation

