

Name : MUZAMIL

COURSE : DLD

Assignment No. 5

QUESTION # 1

(i) $X = \bar{A}[AB + C(D+E)]$ Solve by Nand and nor

Soln:

$$\bar{X} = X$$

$$\therefore X = \bar{A}[B + C(D+E)]$$

Simplify expression


$$X = \bar{A}B + \bar{A}CD + \bar{A}CE \rightarrow (1)$$

$$X = (\bar{A}B)(\bar{A}CD)(\bar{A}CE) \rightarrow (2)$$


$$X = (A + \bar{B})(A + \bar{C} + \bar{D})(A + \bar{C} + E)$$

$$X = (A + \bar{B}) + (A + \bar{C} + \bar{D}) + (A + \bar{C} + E) \rightarrow (3)$$

implementing by using Nand using eq (2)

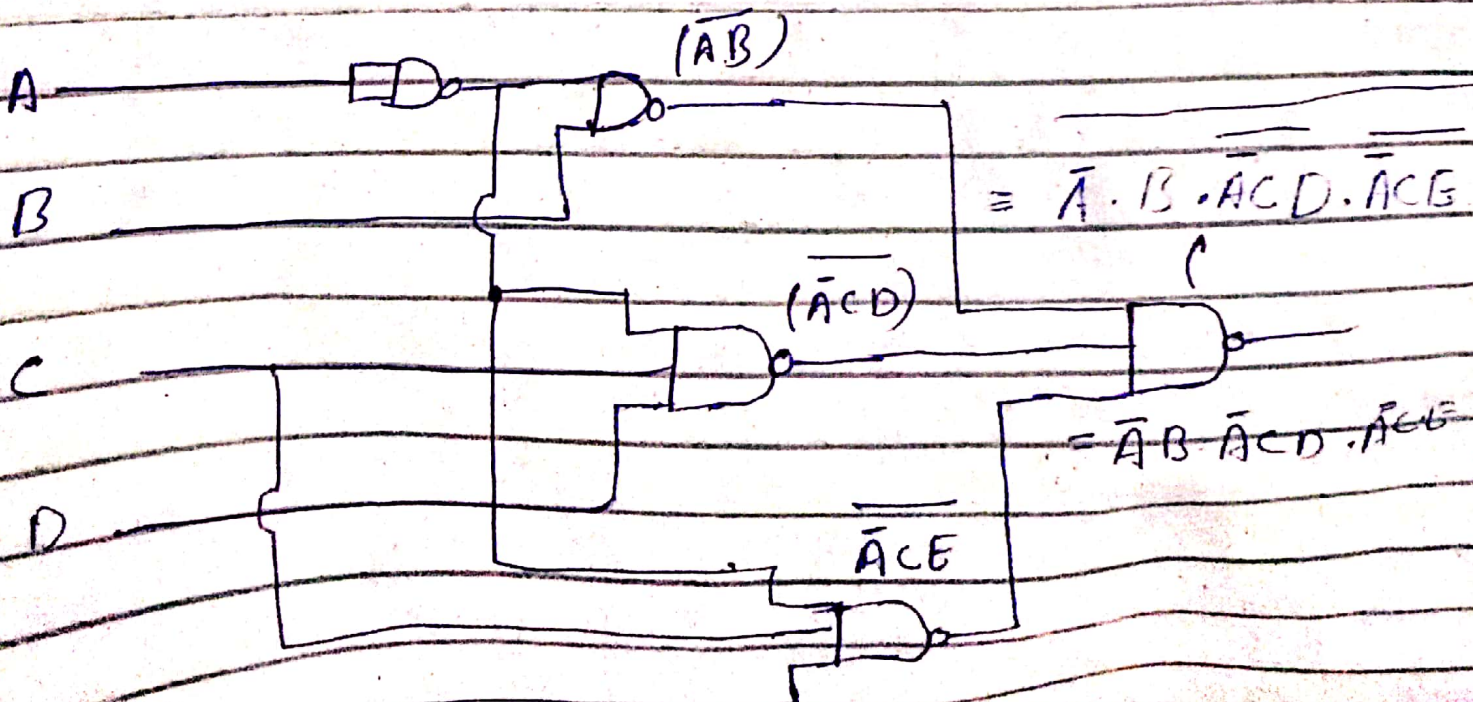


BF using NOR:

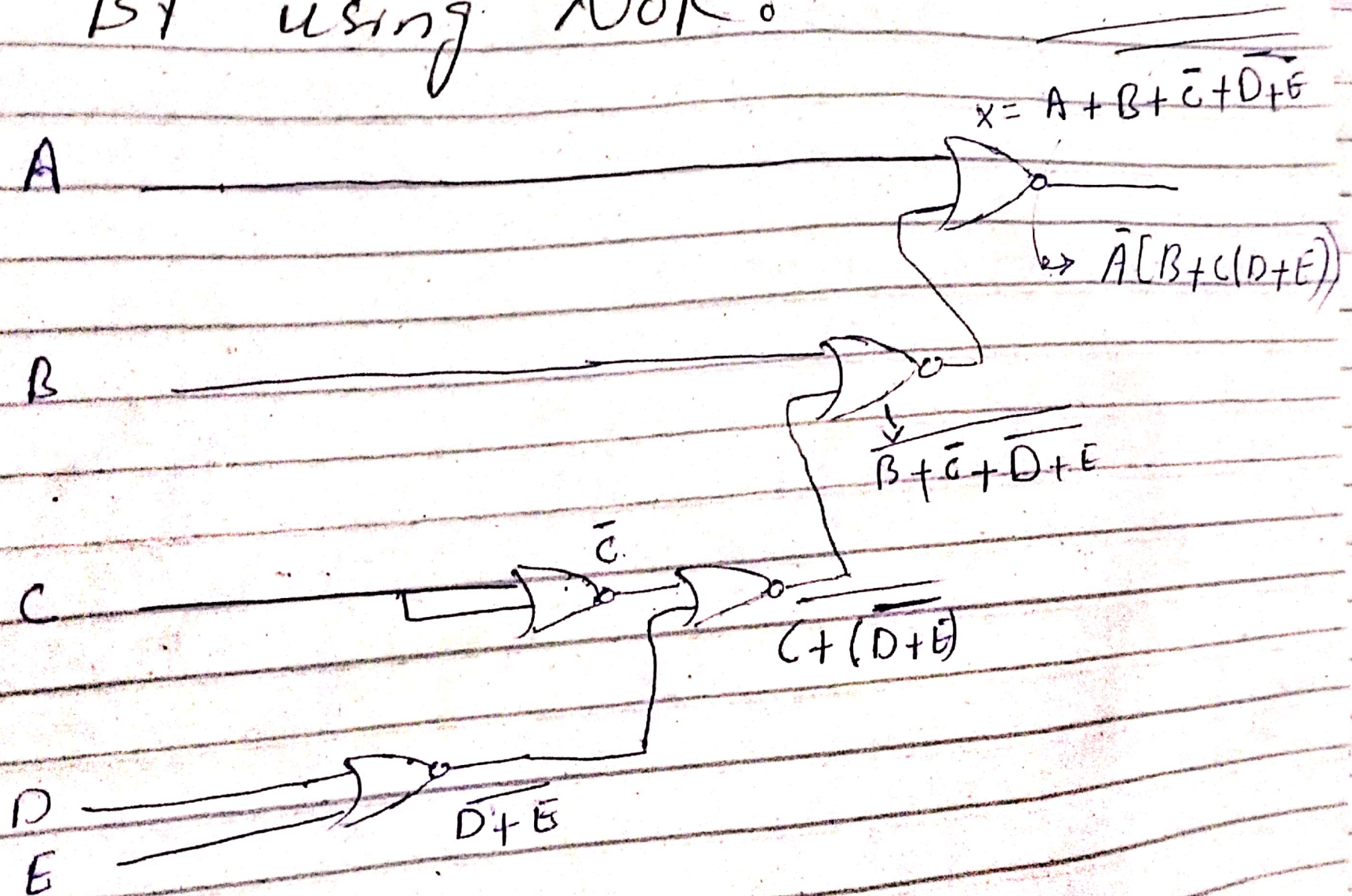

Question #2

(a)


Nand:-

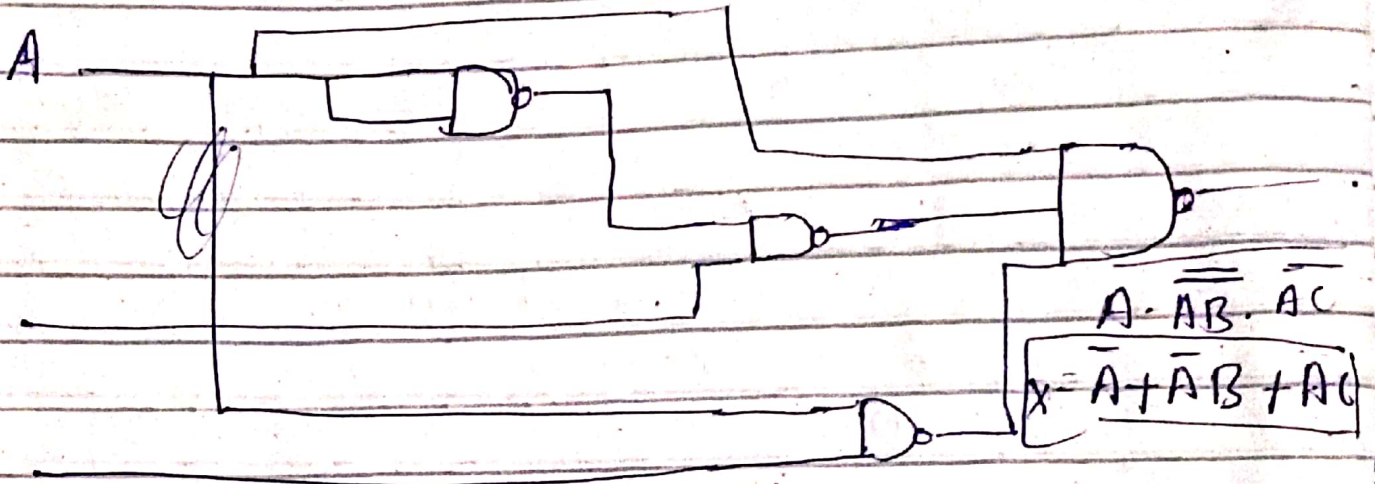

NOR:

Simplifying equation

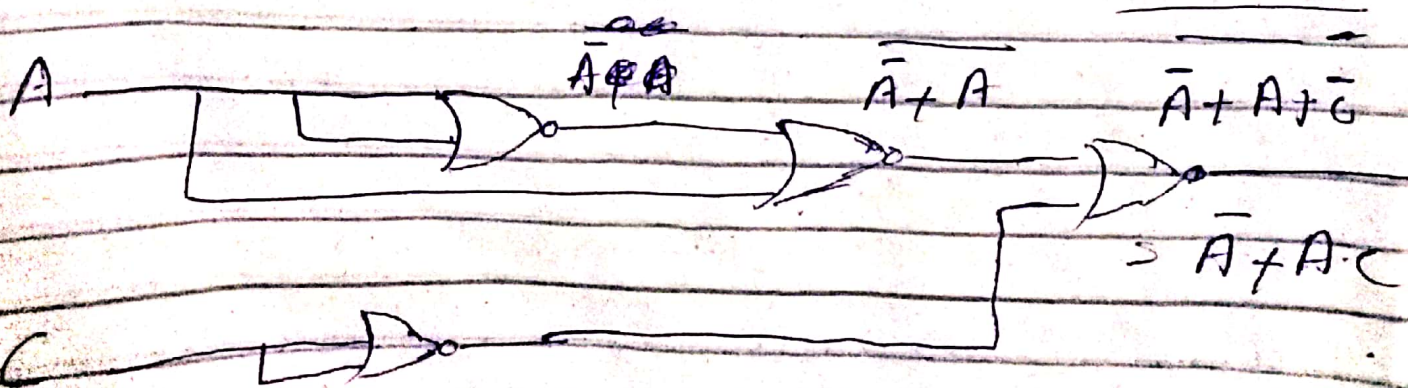
$$\begin{aligned} & \bar{A} + \bar{A}B + AC \\ &= \bar{A}(1+B) + AC \\ & \quad \bar{A} + AC \end{aligned}$$




Question # 2

(b)

Nand

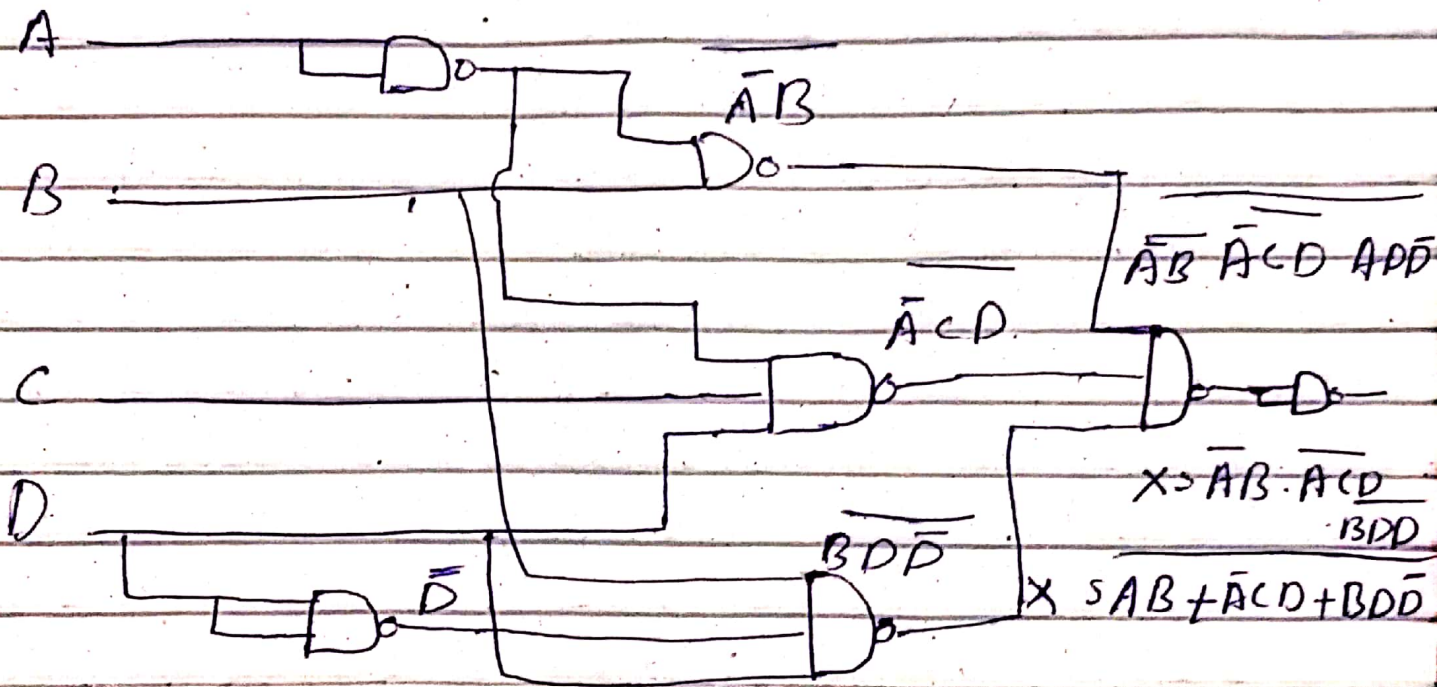

By using NOR

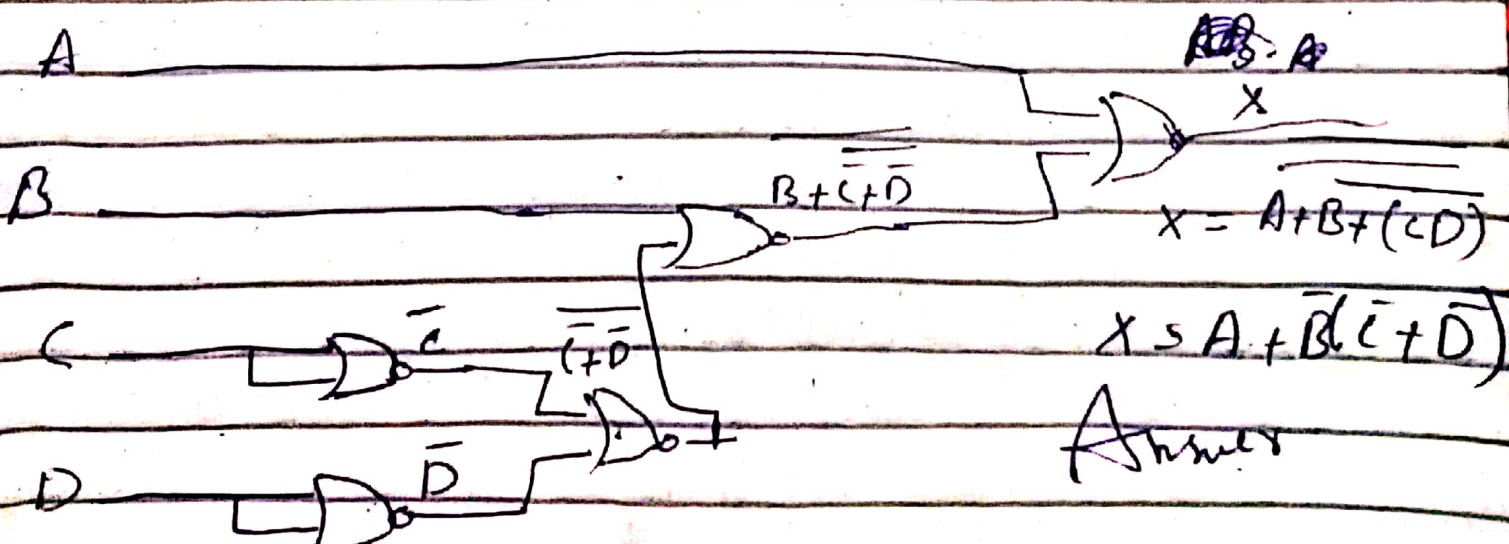

Answer


Question # 3

Q3# How J-K FlipFlop have Solved invalid Condition?

Answer- J-K FlipFlop is with addition of clock input circuitry when Both J and K are "1" the invalid Condition takes place. Thus to prevent invalid Condition clock is introduced.

Question # 9

Problem #16

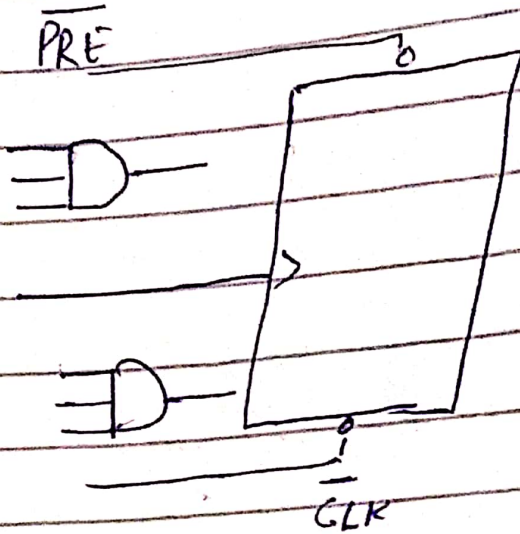

$$J_1 = 1010011, \quad J_2 = 0111010, \quad J_3 = 1111100$$

$$K_1 = 0001110, \quad K_2 = 1101100, \quad K_3 = 1010101$$

Resultant of J from And gate

$$J_1 = 1010011 \quad \text{use And gate}$$

$$J_2 = 0111010$$

$$J_3 = 1111000$$

$$J = 0010000$$

Resultant of K_1, K_2, K_3 From And gate

$$K_1 = 0001110$$

$$K_2 = 1101100$$

$$K_3 = 1010101$$

$$K = 0000100$$

Applying truth table for
Positive triggered edge

$$\begin{array}{r} J \quad 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \\ K \quad 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \\ \hline Q \quad 0 \ 0 \ 1 \ 0 \ 0 \ 0 \end{array}$$

Q = 0 0 1 1 0 0 0 Answer

Problem #1

CLK =

$J_1 =$

$J_2 =$

$J_3 =$

$K_1 =$

$K_2 =$

$K_3 =$

$Q =$