

Lab 6

To Demonstrate the Working of Binary Subtractor

Note: You may draw all the logic diagrams with hand and paste the pictures here or on logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable.

Tasks

1. Construct a logic circuit for half and full subtractor with the help of truth table/Boolean expression. Also write the Boolean expression for output(s).

Half Subtractor

- a) Truth Table

Muzamil / P20-0108 / 2D-1

Half Adder


Truth table

A	B	D	B ₀
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

b) Boolean Expression (Simplified)


Expression
 $D = A \oplus B$
 $B_0 \text{ is } \bar{A}B$

c) Logic Diagram

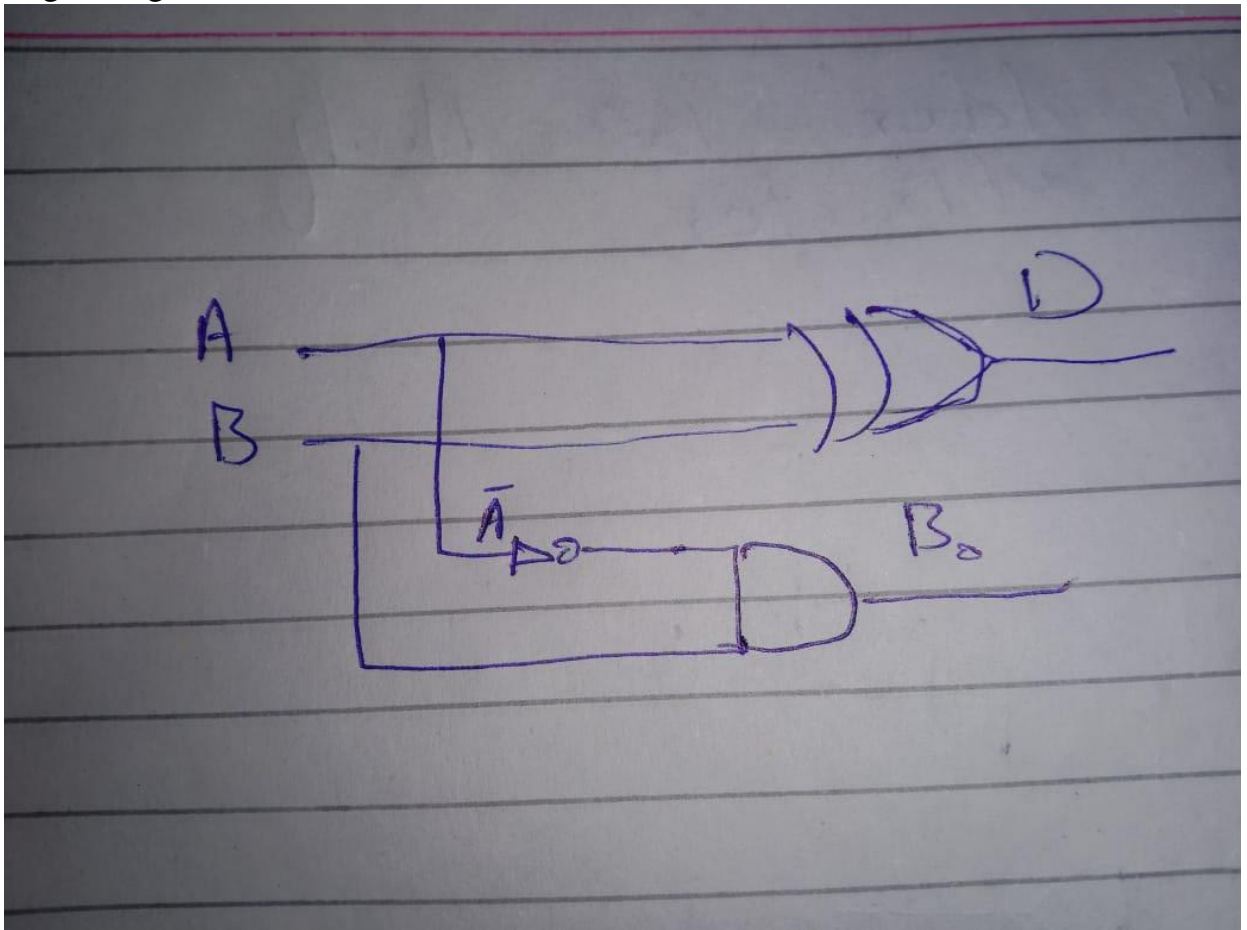


d) Software Simulation ([Show here your results for each combination that gives a high output](#))

Inputs are 1 and 0

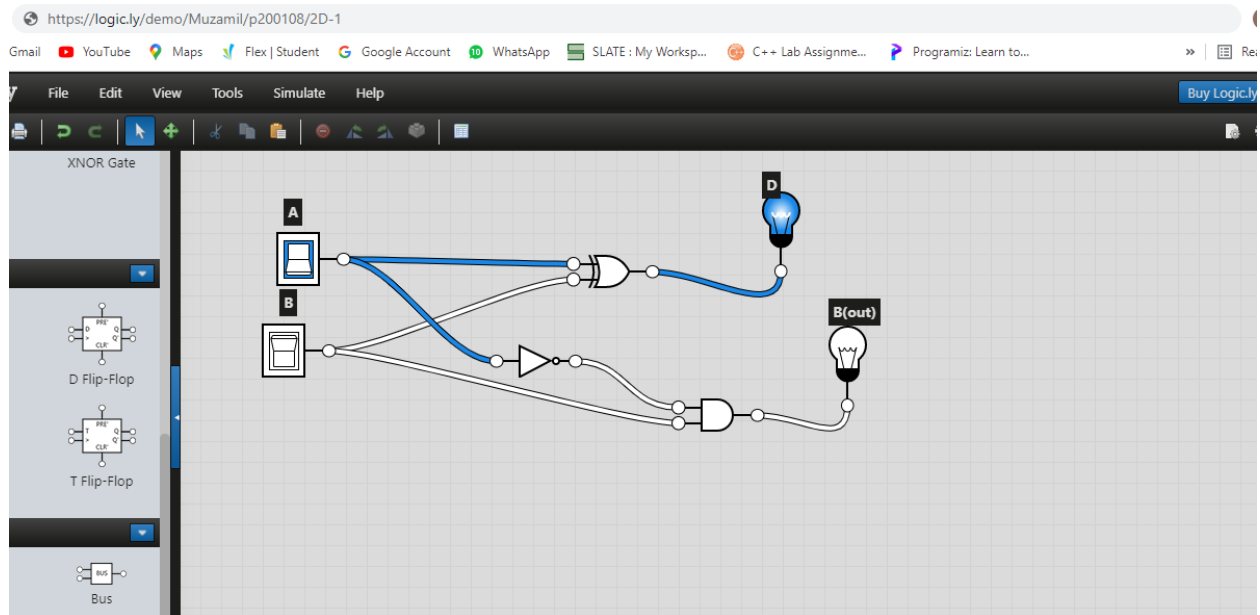

InPUTS ARE 0 AND 1

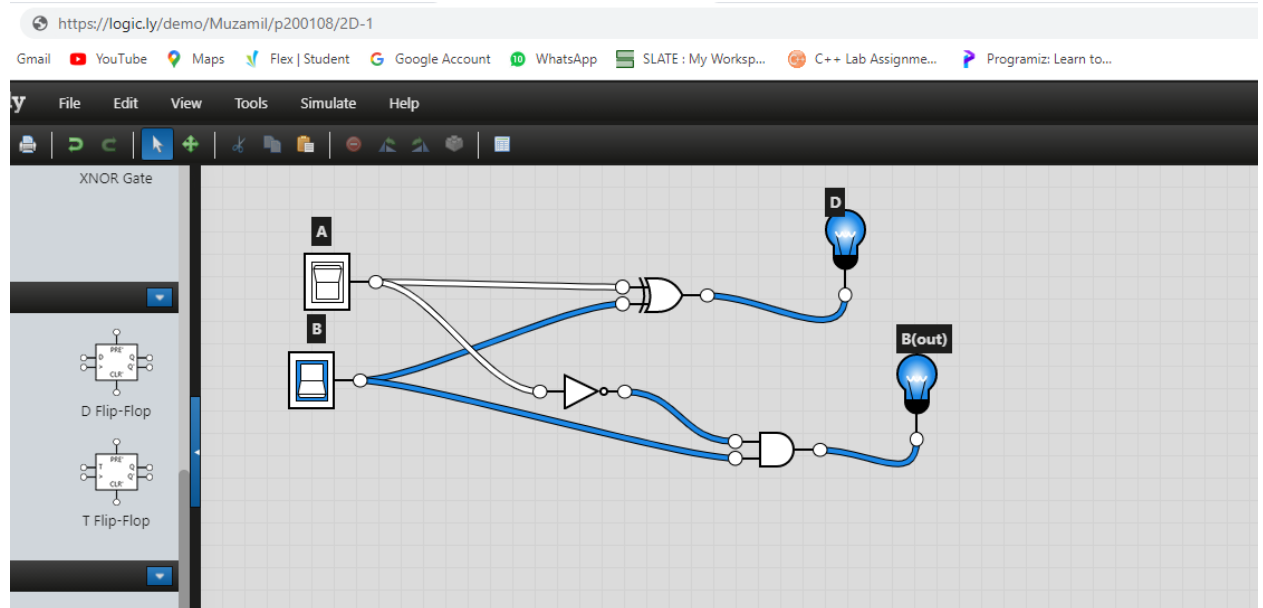

Full Subtractor

a) Truth Table

Full Subtractor

Truth table

A	B	b_{in}	D	b_o
0	0	0	0	0
0	0	1	1	1
0	1	1	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

b) Boolean Expression (Simplified)


Boolean expression

$$\begin{aligned}
 D &= \bar{A}\bar{B}b\bar{in} + \bar{A}Bb\bar{in} + A\bar{B}b\bar{in} + ABb\bar{in} \\
 &= \bar{A}(\bar{B}b\bar{in} + Bb\bar{in}) + A(\bar{B}b\bar{in} + Bb\bar{in}) \\
 D &= \bar{A} \oplus B \oplus b\bar{in}
 \end{aligned}$$


$$\begin{aligned}
 B_{out} &= \bar{A}Bb\bar{in} + \bar{A}Bb\bar{in} + \bar{A}Bb\bar{in} + ABb\bar{in} \\
 &= \bar{A}B(b\bar{in} + b\bar{in}) + b\bar{in}(A\bar{B} + AB) \\
 B_{out} &= \bar{A}B + b\bar{in}(A \oplus B) \\
 B_{out} &= A'B + Bb\bar{in} + A'B\bar{in}
 \end{aligned}$$

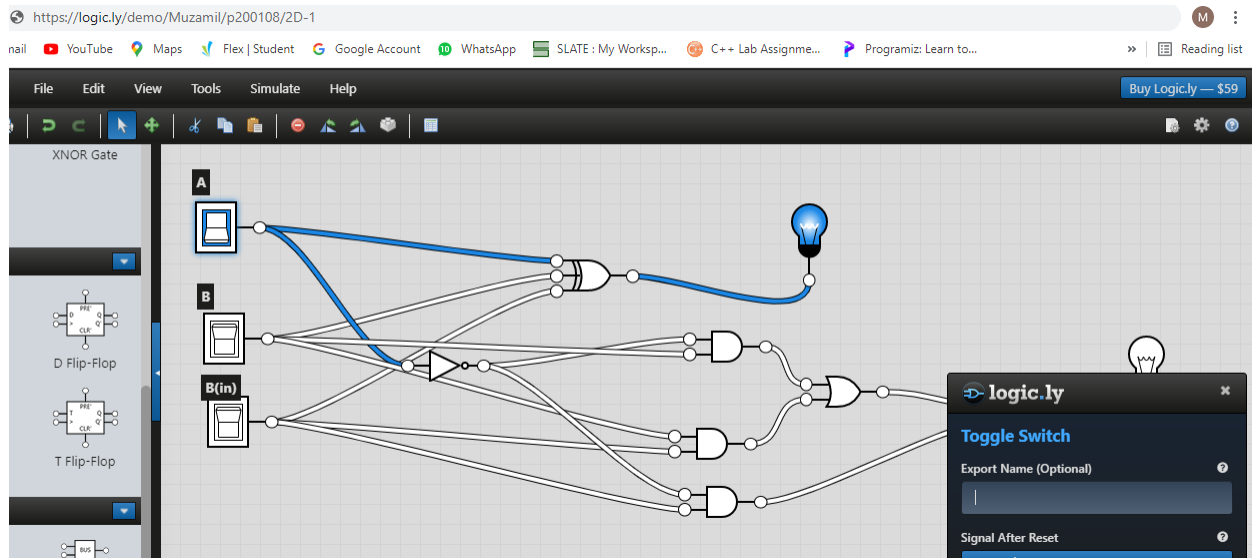c) Logic Diagram

Inputs are 100 and output is 1 and Bout is 0



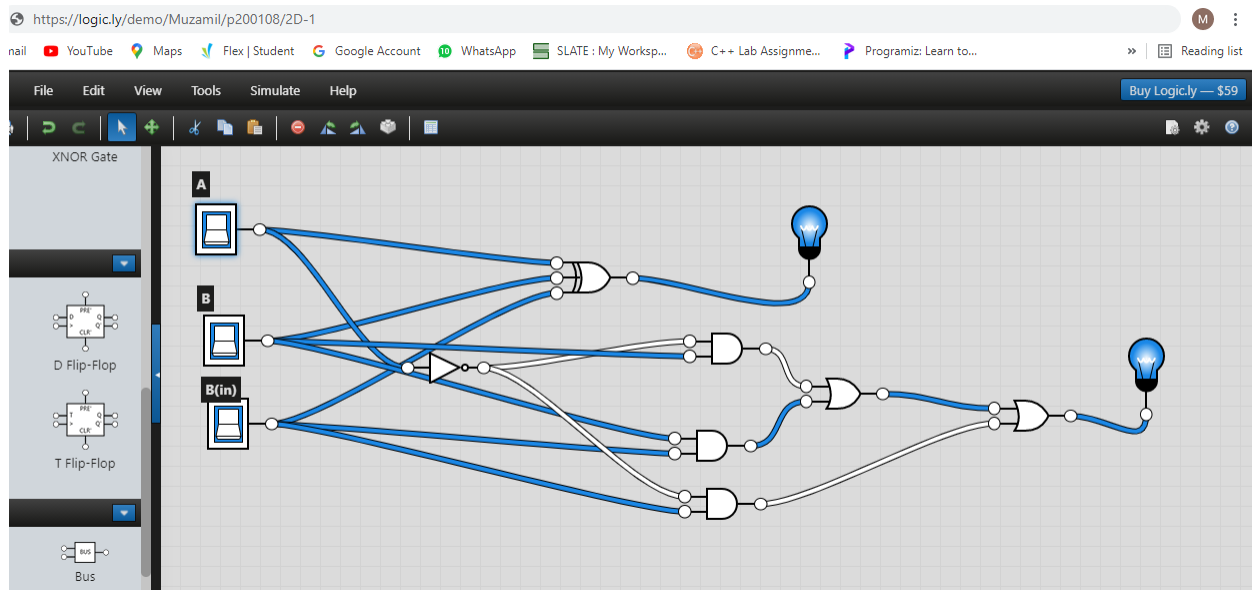
Inputs are 111 and output is 1 and Bout is also 1



2. A full subtractor can be implemented using 2-half subtractors.


Demonstrate the logic diagram for the said circuit. Simulate your circuit for the verification of results.

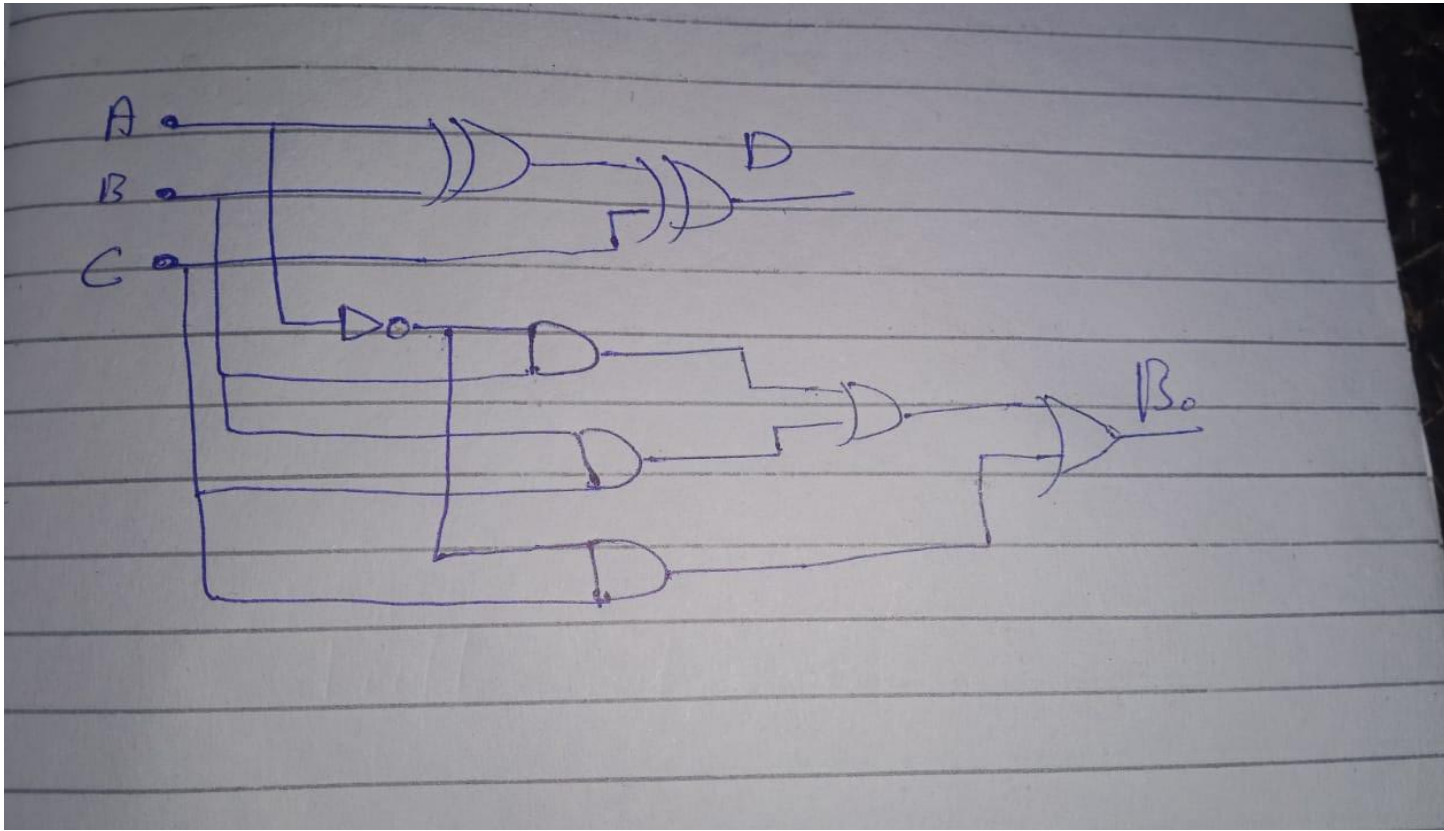a) Logic Diagram of Full Subtractor using 2-Half Subtractor




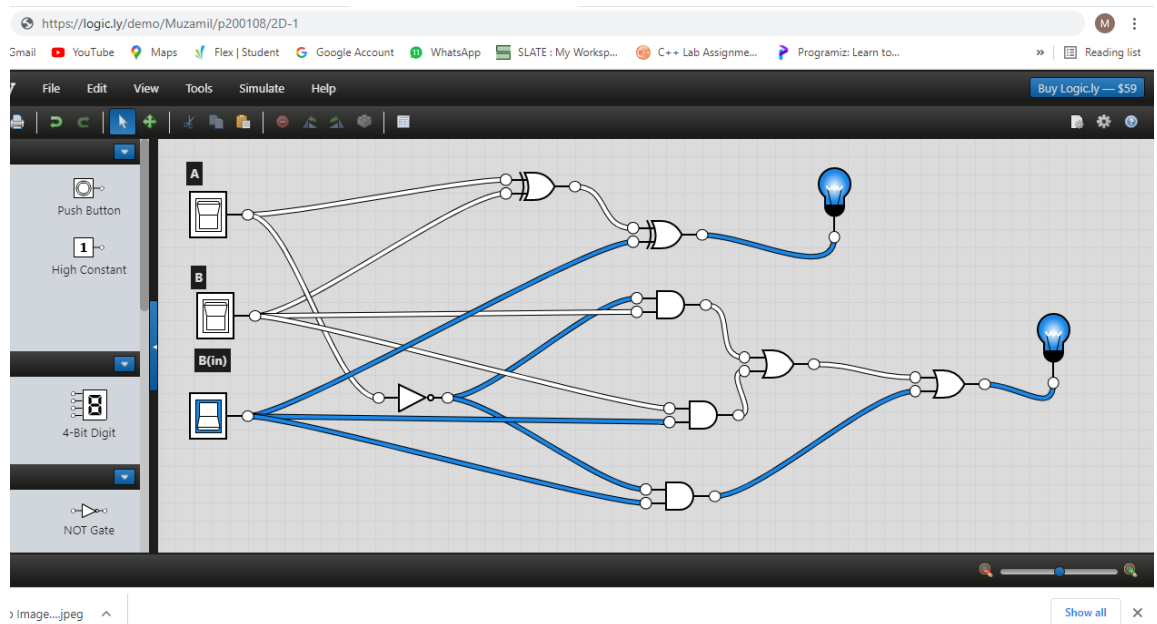b) Software Simulation (Show here your results for each combination that gives a high output)


Inputs are 001 and output is 1 and Bout is 1



Inputs are 100 and output is 1

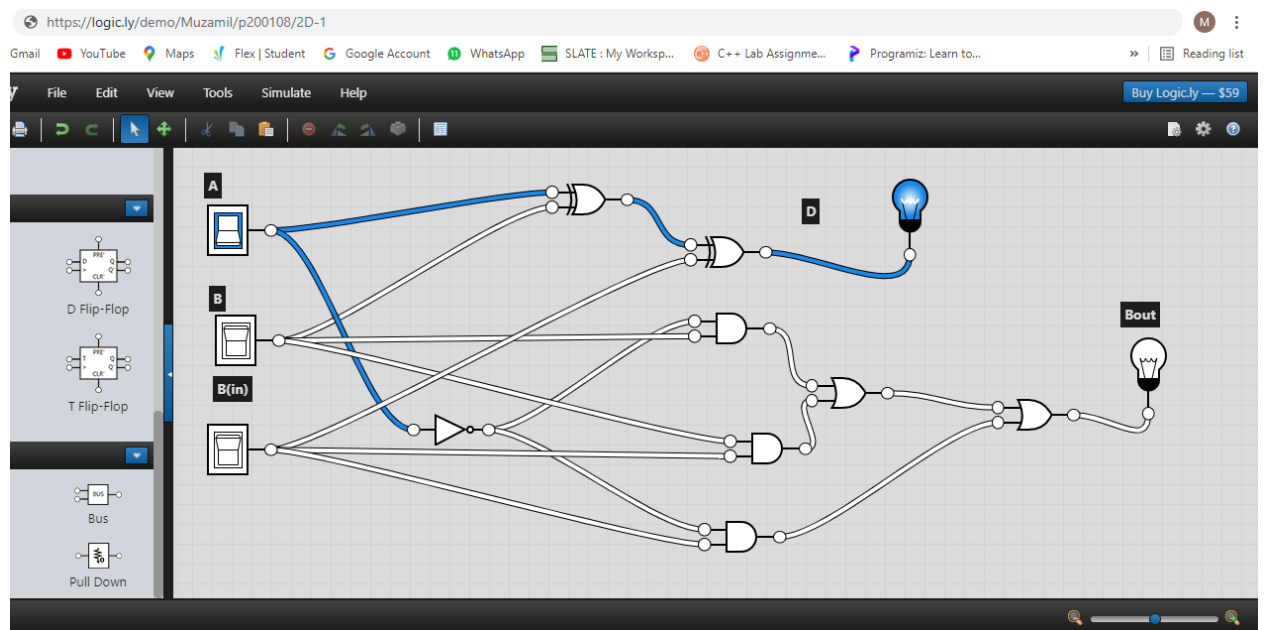

Inputs are 1 1 1 and output is 1

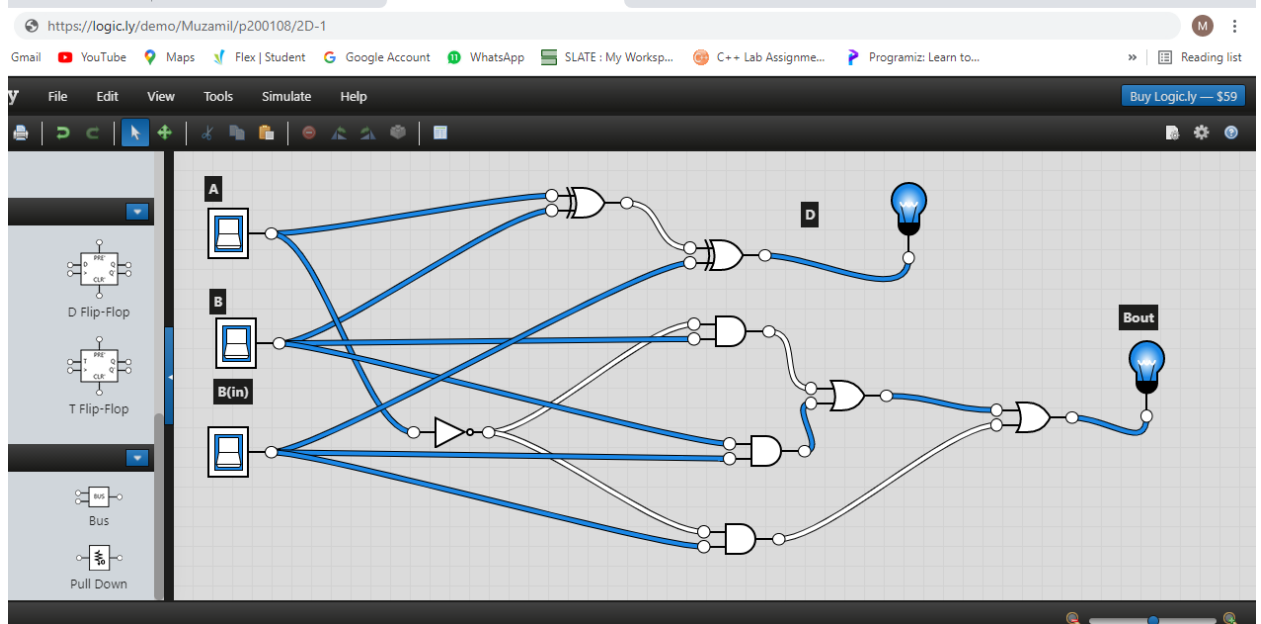

Muzamil

P200108

Lab Task # 6

2D-1